

## Current Electricity - I

**Current:** Rate of flow of charge;


Instantaneous Current

$$I = \frac{Q}{t} \quad 1A = \frac{1C}{1s} = 1Cs^{-1}$$

$$I_{inst} = \lim_{\Delta t \rightarrow 0} \frac{\Delta Q}{\Delta t} = \frac{dQ}{dt}$$

If  $n$  electrons pass through the cross section of a conductor in time  $t$ , then total **charge** passed through the conductor is  $Q = n \times e$


$$\text{Current } I = \frac{ne}{t}$$

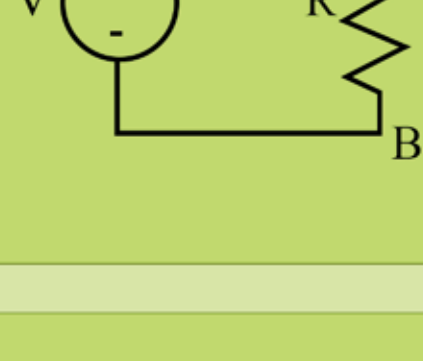

Ohm's Law :  $V = IR \Rightarrow R = \frac{V}{I}$

$$1\Omega = \frac{1V}{1A}$$

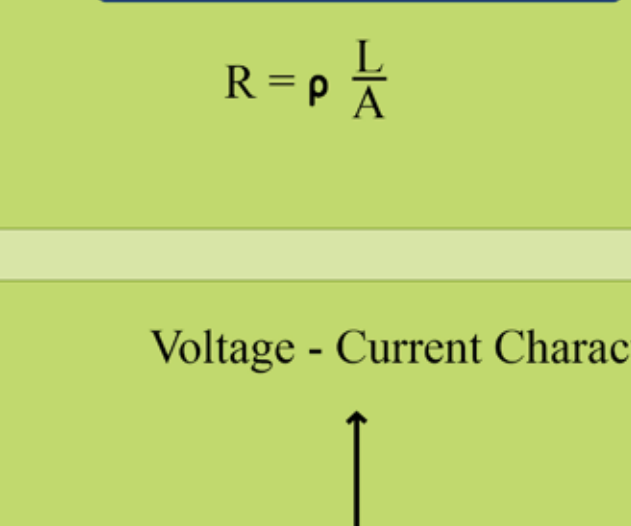Resistance (R) : Obstruction offered to the flow of current by the conductor.




$$R = \rho \frac{L}{A}$$

For a Cylindrical Wire

$$\rho = \frac{1}{\sigma} = \frac{(\pi r^2) R}{L} \Omega m$$

$$\text{Current Density } j = \frac{I}{A} = \sigma E$$

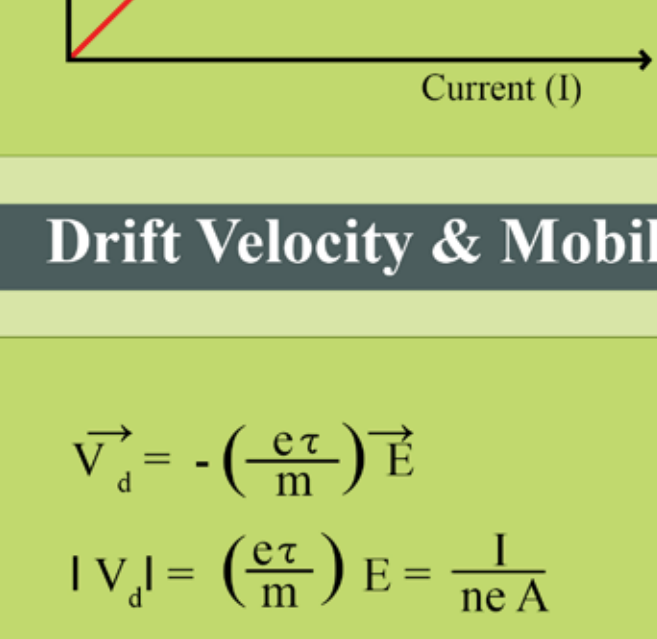Voltage - Current Characteristics - Ohm's Law Graph



$\vec{V}_d = - \left( \frac{e\tau}{m} \right) \vec{E}$

$$I V_d = \left( \frac{e\tau}{m} \right) E = \frac{I}{neA}$$


$V_d$  = drift velocity of free electrons

$\tau$  = average relaxation time

$n$  = number of free electrons

$$\text{Mobility } (\mu) = \frac{I V_d I}{E} = \frac{e\tau}{m}$$
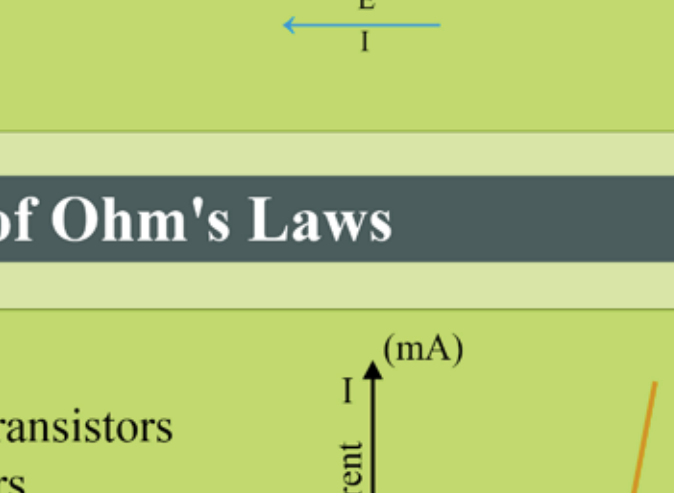
$$\text{S. I unit of } \mu \text{ is } \frac{m^2}{Vs}$$



## Limitations of Ohm's Laws

Ohm's Law is NOT applicable to

a) Unilateral Networks: Diodes, Transistors

b) Non - linear elements: Thyristors

For Non - Ohmic Conductors:

V is not proportional to I



Diode

## Current Electricity - II

### Resistivities of Various Materials

Resistivity of Metals - Lowest

Semiconductors - Moderate

Insulators - Highest

### Temperature Dependence Of Resistivity

$$\rho_t = \rho_0 [1 + \alpha (T - T_0)]$$

$\rho_t$  - Resistivity at a temperature T.

$\rho_0$  - Resistivity at a reference temperature  $T_0$ .

$\alpha$  - temperature coefficient of resistivity


( $\alpha > 1$  for Metals or Conductors)

Note : With increase in temperature,

Resistance of Conductors Increase (&

Resistance of Semiconductors and Insulators decrease

### Colour Coding of Resistor

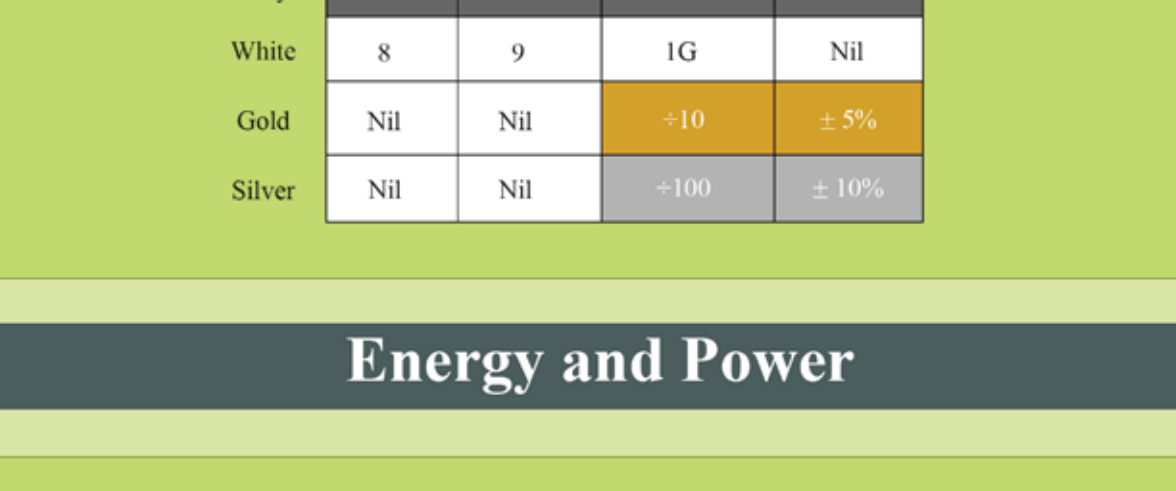

	First Digit	Second Digit	Multiplier	Tolerance
Black	Nil	0	1	Nil
Brown	1	1	10	$\pm 1\%$
Red	2	2	100	$\pm 2\%$
Orange	3	3	1000	$\pm 3\%$
Yellow	4	4	10000	$\pm 4\%$
Green	5	5	100000	$\pm 0.5\%$
Blue	6	6	1M	$\pm 0.25\%$
Violet	7	7	10M	$\pm 0.10\%$
Grey	8	8	100M	$\pm 0.05\%$
White	8	9	1G	Nil
Gold	Nil	Nil	$\div 10$	$\pm 5\%$
Silver	Nil	Nil	$\div 100$	$\pm 10\%$

### Energy and Power


Power dissipated in a resistor  $P = I^2 R = V^2 / R = IV$

Energy dissipated in a resistor in a time interval  $\Delta t$  is


$$\Delta W = IV \cdot \Delta t = I^2 R \cdot \Delta t$$

(SI unit of Power is Watt & Energy is Joule)
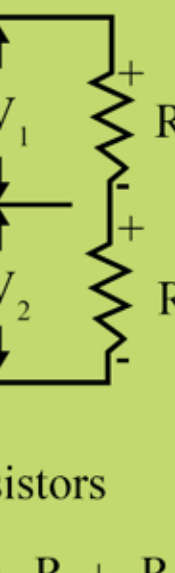
$$\text{Power dissipated in the transmission wires } P_c = \frac{P^2 R_c}{V^2}$$




### Combination of Resistors

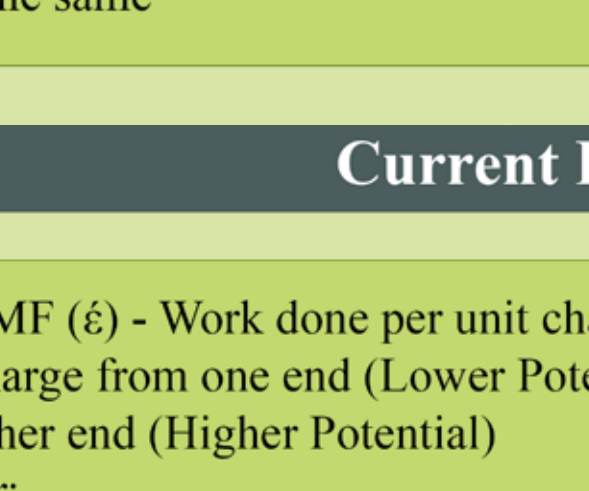

Parallel resistors

$$\frac{1}{R_{equivalent}} = \frac{1}{R_1} + \frac{1}{R_2}$$

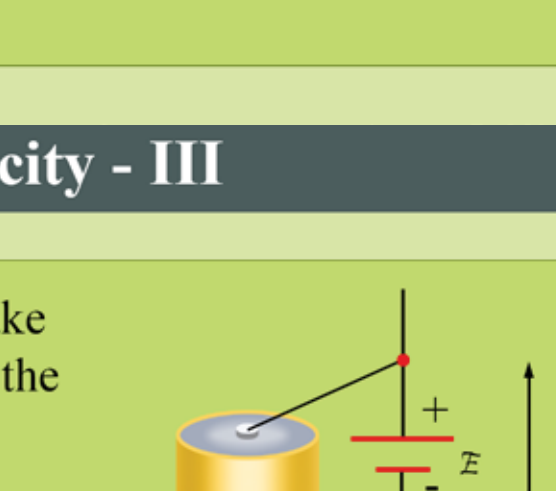In Parallel : The Voltage drop across each of the branches is the same



Series resistors

$$R_{equivalent} = R_1 + R_2$$


In Series : The current is the same at each resistor

## Current Electricity - III

EMF ( $\epsilon$ ) - Work done per unit charge to take charge from one end (Lower Potential) to the other end (Higher Potential)

Or:

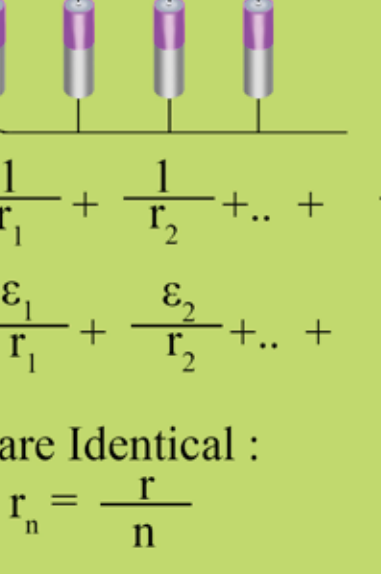EMF ( $\epsilon$ ) - The potential difference between the positive And negative electrodes in an open circuit,



### Combination of Cells

#### Series

$$\epsilon_{eq} = \epsilon_1 + \epsilon_2 + \dots + \epsilon_n$$

$$r_{eq} = r_1 + r_2 + \dots + r_n$$

If Cells are Identical :

$$\epsilon_{eq} = n\epsilon \text{ \& } r_{eq} = nr$$


#### Parallel

$$\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}$$

$$\frac{\epsilon_{eq}}{r_{eq}} = \frac{\epsilon_1}{r_1} + \frac{\epsilon_2}{r_2} + \dots + \frac{\epsilon_n}{r_n}$$

If Cells are Identical :
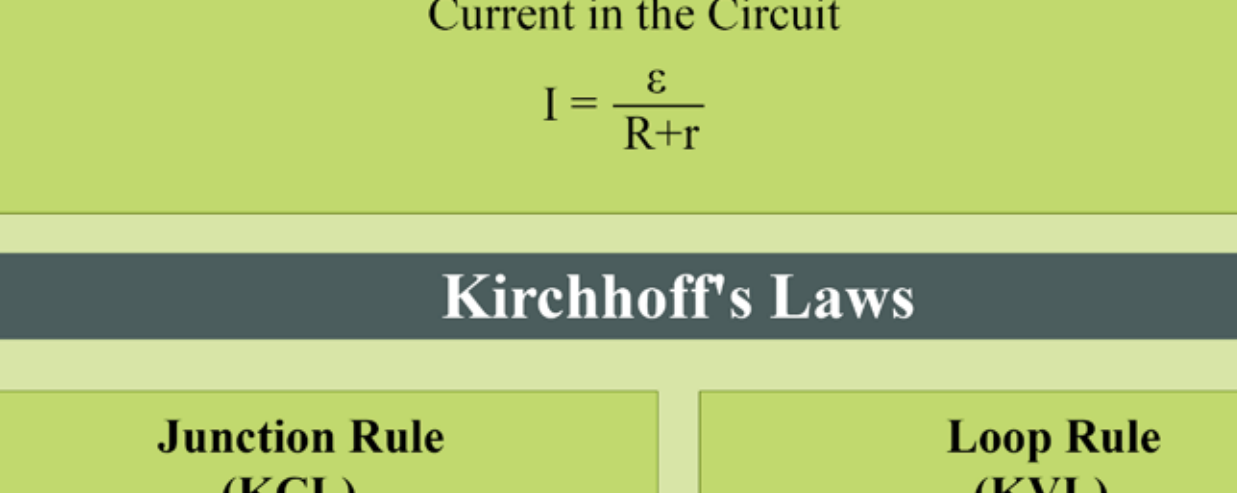
$$\epsilon_n = \epsilon \text{ \& } r_n = \frac{r}{n}$$



Current in the Circuit

$$I = \frac{\epsilon}{R + r}$$

## Kirchhoff's Laws


### Junction Rule (KCL)



$$\sum i = 0$$


$$i_1 + i_3 = i_2 + i_4$$

### Loop Rule (KVL)

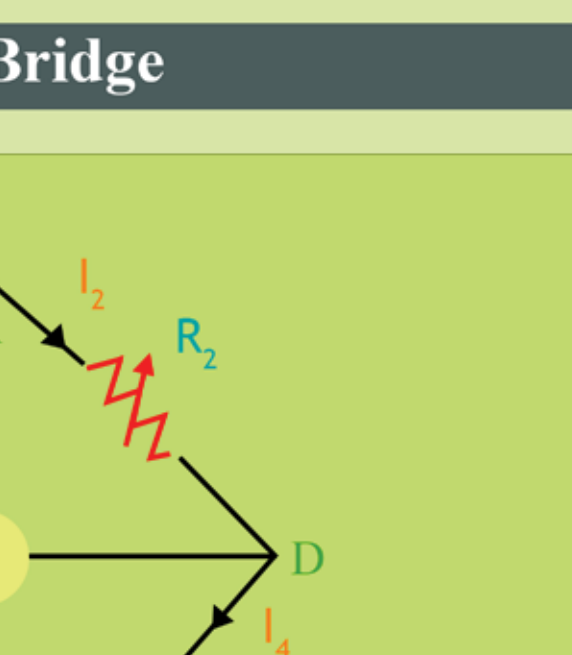

$$\sum V = 0$$

## Wheatstone Bridge

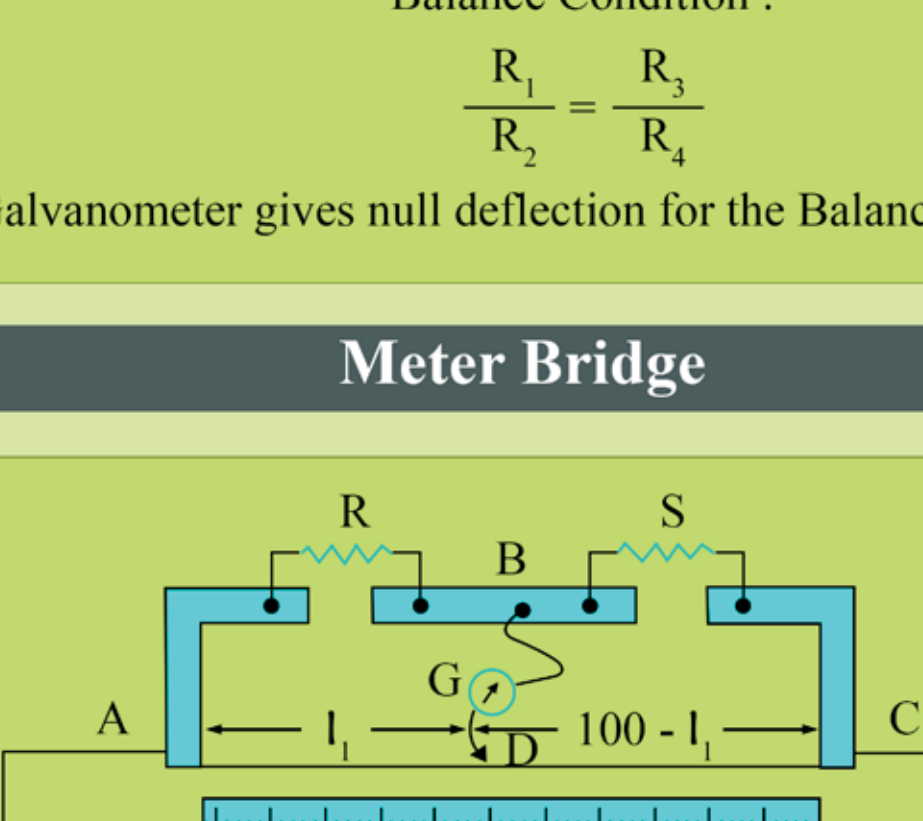


Balance Condition :

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

Note : Galvanometer gives null deflection for the Balance Condition

## Meter Bridge

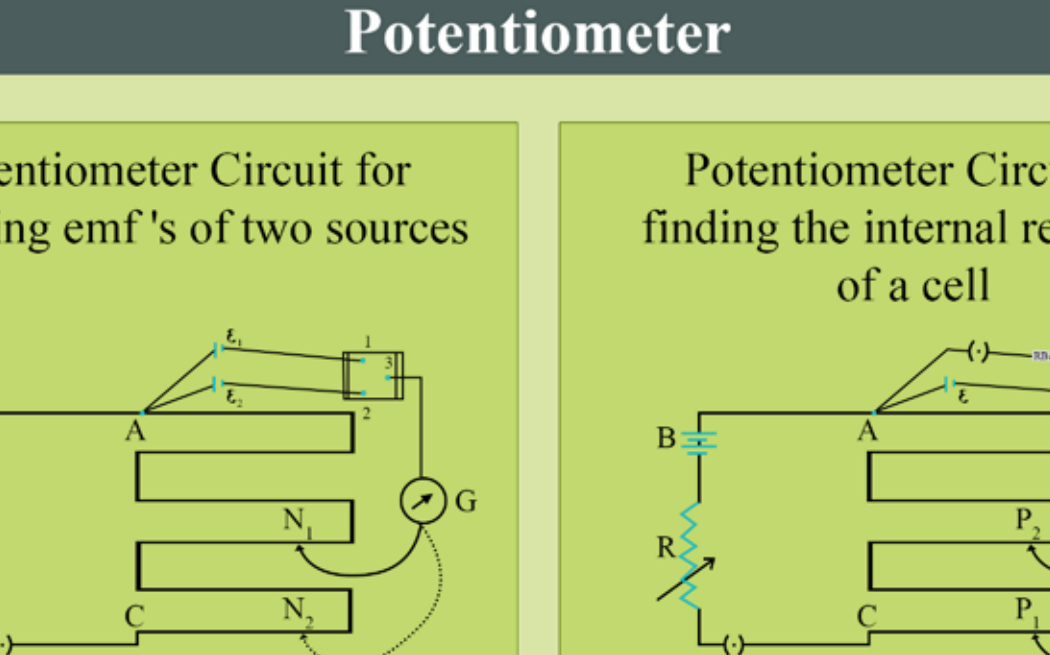

Balance Condition :

$$\frac{R}{S} = \frac{l_1}{(100 - l_1)}$$

## Potentiometer

Potentiometer Circuit for comparing emf's of two sources



$$\frac{\epsilon_1}{\epsilon_2} = \frac{l_1}{l_2}$$

Potentiometer Circuit for finding the internal resistance of a cell



$$r = R \left[ \frac{l_1}{l_2} - 1 \right]$$