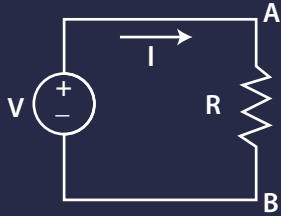


# ELECTRICITY

If  $n$  electrons pass through the cross section of a conductor in time  $t$ , then total charge passed through the conductor is  $Q = n \times e$ .


$$1 e = 1.6 \times 10^{-19} C ; 1 C = 6.25 \times 10^{18} e$$

- **Current** : Rate of flow of charge  $I = \frac{Q}{t}$   $1 A = \frac{1 C}{1 s} = 1 C s^{-1}$
- **Potential at a point** : Amount of work done per unit charge in bringing a positive charge from infinity to that point ;  $V = \frac{W}{Q}$   $1 V = 1 J C^{-1}$



Potential Difference :  $V_A - V_B = \frac{W}{Q}$

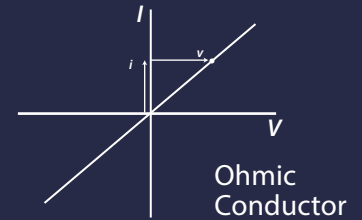Ohm's Law :  $V = IR \Rightarrow R = \frac{V}{I}$   $1 \Omega = \frac{1 V}{1 A}$




- **Resistance** : Obstruction offered to the flow of current by conductor.

$$R = \rho \frac{l}{A} \quad \text{Resistivity } \rho = \frac{\pi r^2 R}{l} \Omega m$$

Ohm's Law is NOT applicable to

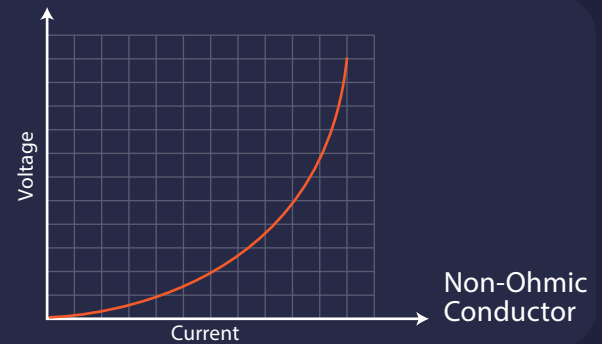- Unilateral networks : Diodes, Transistors
- Non-linear elements : Thyristors




## Band Resistor



	First Digit	Second Digit	Multiplier	Tolerance
Black	Nil	0	1	Nil
Brown	1	1	10	±1%
Red	2	2	100	±2%
Orange	3	3	1000	±3%
Yellow	4	4	10000	±4%
Green	5	5	100000	±0.5%
Blue	6	6	1M	±0.25%
Violet	7	7	10M	±0.10%
Gray	8	8	100M	±0.05%
White	9	9	1G	Nil
Gold	Nil	Nil	×10	±5%
Silver	Nil	Nil	×100	±10%

## Combination of Resistances

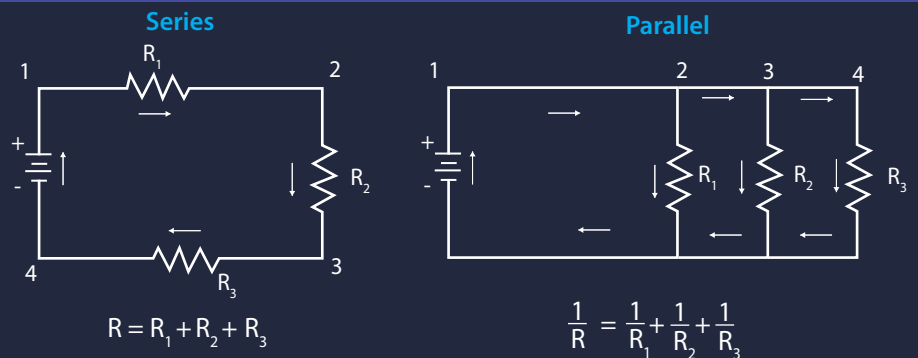

Heating effect of current depends on:

- Amount of current passing,  $I^2$
- Resistance of wire,  $R$
- Time for which current flows,  $t$

$$H = I^2 R t$$


Joule

$$\text{Power } P = VI = I^2 R = \frac{V^2}{R} \text{ watts}$$

## Applications



## Kirchoff's 1st Law

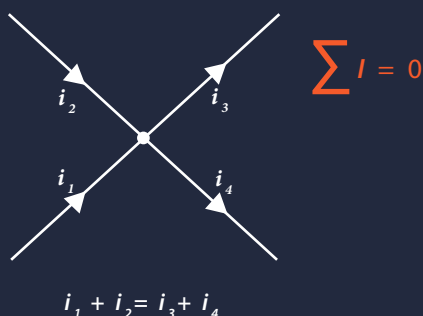

## Kirchoff's 2nd Law

